



## 1.1 & 1.2

A **BOOLEAN EXPRESSION** CAN BE SYNTHESIZED FROM ANY TRUTH TABLE.


A **LOGIC GATE** IS A PHYSICAL DEVICE THAT IMPLEMENTS A SIMPLE **BOOLEAN FUNCTION**.



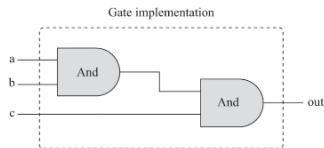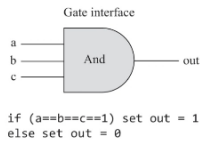→ **INTERFACE** (WHAT THE GATE IS SUPPOSED TO DO)



a	b	out
0	0	0
0	1	1
1	0	1
1	1	0

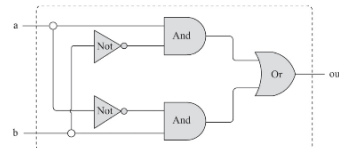

**THREE-WAY AND**

**XOR**

→ **IMPLEMENTATION**

(HOW TO BUILD THE GATE'S FUNCTIONALITY)

1.4 **MULTIPLEXER** WORKS SIMILARLY TO AN "IF":

IT TAKES TWO INPUT BITS, **a** AND **b**, AND INTERPRETS THEM AS **DATA BITS**.

THE THIRD INPUT BIT, NAMED **sel**, IS THE **SELECTION BIT**.

IT OUTPUTS EITHER **a** OR **b**.

**DEMULTIPLEXER** IS THE OPPOSITE:

TAKES A SINGLE INPUT VALUE AND PASSES IT EITHER TO **A** OR **B**, DEPENDING ON THE **SELECTOR**.

**MULTI-BIT GATE**: AN **N-BIT GATE** APPLIES THE **BOOLEAN OPERATION** IT HOLDS TO EVERY ONE OF THE BITS IN ITS **N-BIT INPUT**.

EX. **16 BIT NOT GATE**:

FOR  $i = 0 \dots 15$   $OUT[i] = NOT(IN[i])$

**MULTI-WAY GATE**:

EX. AN **M-WAY OR GATE** OUTPUTS **1** WHEN AT LEAST ONE OF ITS **M INPUT BITS** IS **1**, AND **0** OTHERWISE.

1.5 **NOT**: CAN BE IMPLEMENTED USING A SINGLE **NAND**

1.6 **ORDER**:

**AND**: NOT AND NAND

**OR**: AND AND NOT

**XOR** AND, NOT, AND OR